



Computer Engineering

Electrical Engineering Department

Third Stage


Instructor: Asst. Lecturer

Adnan Ali Abdullah


Maximum-Mode Interface

- ❑ The maximum-mode configuration is mainly used for implementing a ***multiprocessor/coprocessor system environment*** which means that multiple processor exist in the system and each processor execute its own program.
- ❑ 8086 μ P does not directly provide all the signals that are required to control the memory, I/O and interrupt interfaces.
- ❑ $\overline{S_2} \overline{S_1} \overline{S_0}$ are input to the external bus controller device (**8288 Bus Controller**) , the bus controller generates the timed command and control signals.

Status Inputs			CPU Cycles	8288 Command
$\overline{S_2}$	$\overline{S_1}$	$\overline{S_0}$		
0	0	0	Interrupt Acknowledge	$\overline{INTA}$
0	0	1	Read I/O Port	$\overline{IORC}$
0	1	0	Write I/O Port	$\overline{IOWC}, \overline{AIOWC}$
0	1	1	Halt	None
1	0	0	Instruction Fetch	$\overline{MRDC}$
1	0	1	Read Memory	$\overline{MRDC}$
1	1	0	Write Memory	$\overline{MWTC}, \overline{AMWC}$
1	1	1	Passive	None

 


8288 Bus Controller

 

System Clock

- To synchronize the internal and external operations of the microprocessor a clock (CLK) input signal is used. The CLK can be generated by the 8284 clock generator IC.
- The 8086 μ P is manufactured in three speeds: 5 MHz, 8 MHz and 10 MHz
- For 8086 μ P, we connect either a 15-, 24- or 30-MHz crystal between inputs X1 and X2 inputs of the clock chip (see Fig. 8-11). The fundamental crystal frequency is divided by 3 within the 8284 to give either a 5-, 8- or 10-MHz
- clock signal, which is directly connected to the CLK input of the 8086 μ P.

 

Bus Cycle and Time States

A bus cycle defines the sequence of events when the MPU communicates with an external device, which starts with an address being output on the system bus followed by a read or write data transfer.


Types of bus cycles:

- Memory Read Bus Cycle
- Memory Write Bus Cycle
- Input / Output Read Bus Cycle
- Input / Output Write Bus Cycle

The bus cycle of the 8086 μ P microprocessor consists of at least four clock periods. These four time states are called T_1 , T_2 , T_3 and T_4 .

Two Basic Memory Operations

 The memory unit supports two fundamental operations: Read and Write. The read operation reads a previously stored data and the write operation stores a value in memory, see the figure below.




Memory Read and write Bus Cycles

The following steps have to be followed in a typical read cycle:


1. Place the address of the location to be read on the address bus.
2. Activate the memory read control signal on the control bus.
3. Wait for the memory to retrieve the data from the address memory location.
4. Read the data from the data bus.
5. Drop the memory read control signal to terminate the read cycle.

The following steps have to be followed in a typical write cycle:

 1. Place the address of the location to be written on the address bus.
2. Place the data to be written on the data bus.
3. Activate the memory write control signal on the control bus.
4. Wait for the memory to store the data at the address location..
5. Drop the memory write control signal to terminate the write cycle.



Memory Read Bus Cycle

 

Memory Write Bus Cycle

Hardware Organization of the Memory Address Space


The 8088 μ P's memory address space as shown in figure below is implemented as single 1 Mbyte memory bank. The 8086 μ P's 1 Mbyte memory address space as shown in figure below is implemented as two independent 512 Kbyte banks:

- ❑ Data bytes associated with an even address (00000, 00002, , FFFFE) reside in the low bank.
- ❑ Data bytes associated with an odd addresses (00001, 00003, , FFFFF) reside in the high bank.


Address bits A1 through A19 select the` location that is to be accessed. They are applied to both banks in parallel. **A0 (BLE)** and bank high enable (**BHE**) are used as **bank-select** signals:

- ❑ **A₀ = 0** causes the low bank to be enabled.
- ❑ **BHE = 0** causes the high bank to be enabled.

 Each of the memory banks provides half of the 8086 μ P's 16-bit data bus. The lower bank transfers bytes of data over data lines D₀ through D₇, while data transfers for a high bank use D₈ through D₁₅.




High and low memory banks of the 8086


 


1Mx8 memory bank of the 8088

 - ❑ The byte transfer operation and word transfer operation of the 8088 μ P is as illustrated in figure below. The byte transfer operation needs one bus cycle, while word transfer operation needs two bus cycles.




Byte transfer by the 8088

  


Word transfer by the 8088

Figure below shows how a byte transfer operation is performed to address X, an even-addressed storage location. A₀ is set to logic 0 to enable the low bank of memory and BHE to logic 1 to disable the high bank. Data are transferred to or from the lower bank over data bus lines D₀ - D₇.

 


Even address byte transfer by the 8086

Figure below shows how a byte transfer operation is performed to an odd addressed storage location such as $X + 1$. A_0 is set to logic 1 and $\overline{BHE}$ to logic 0. This enables the high bank of memory and disables the low bank. Data are transferred over bus lines D_8 through D_{15} . D_8 represents the LSB.

 


Odd address byte transfer by the 8086

Figure below illustrates how an aligned word (at even address X) is accessed. Both the high and low banks are accessed at the same time. Both A_0 and $\overline{BHE}$ are set to 0. This 16-bit word is transferred over the complete data bus D_0 through D_{15} in just one bus cycle.

 

Even address word transfer by the 8086

Figure below illustrates how a misaligned word (at address $X + 1$) is accessed. Two bus cycles are needed. During the first bus cycle, the byte of the word located at address $X + 1$ in the high bank is accessed over D_8 through D_{15} . Even though the data transfer uses data lines D_8 through D_{15} , to the processor it is the low byte of the addressed data word. In the second memory bus cycle, the even byte located at $X + 2$ in the low bank is accessed over bus lines D_0 through D_7 .

 

Input /Output Interface

Input / Output (I/O) devices provide the means by which the computer system can interact with the outside world.

Computers use I/O devices (also called peripheral devices) for two major purposes:

- 1- To communicate with the outside world and,
- 2- Store data.

Devices that are used to communicate like, printer, keyboard, modem. Devices that are used to store data like disk drive. I/O devices are connected to the system bus through **I/O controller** (interface) – which acts as interface between the system bus and I/O devices. The 8086 μ P employs two different types of input/output (I/O): **Isolated I/O** and **Memory-mapped I/O**. These I/O methods differ in how I/O ports are mapped into the 8086's address spaces.

Isolated Input/Output:

The I/O devices are treated separate from memory. I/O ports are organized as bytes of data; the memory address space contains 1M consecutive byte addresses in the range 00000H, through FFFFFH; and the I/O address space contains 64K consecutive byte addresses in the range 0000H through FFFFH as shown in figure below.

The way in which the microprocessor deals with input/output devices is similar to the way in which it deals with memory. The only difference is that just the 16 least significant lines of the bus, AD0 through AD15, are in use (because I/O addresses are 16 bit long), and throughout the bus cycles, the M/IO control signal is set to 0.

 


Figure 8-44 8088/8086 memory and I/O address spaces.

Advantages of Isolated I/O

Complete memory address space available for use by memory.

I/O instructions maximizes the performance.

Disadvantage of Isolated I/O

All inputs/outputs must take place between an I/O port and accumulator register.

Memory Mapped I/O

The address space dedicated to I/O devices is a part of the memory. Addresses

E0000H - E0FFFH → 4096 memory locations are assigned to I/O ports.

E0000H, E0001H, and E0002H correspond to byte-wide ports 0,1, and 2.

E0000H and E0001H correspond to word-wide port 0 at address E0000H.

Advantages of memory mapped I/O

I/O transfers can take place between I/O port and any of the registers.

Disadvantage of memory mapped I/O

Memory instructions perform slower.

Part of the memory address space cannot be used to implement memory.

