
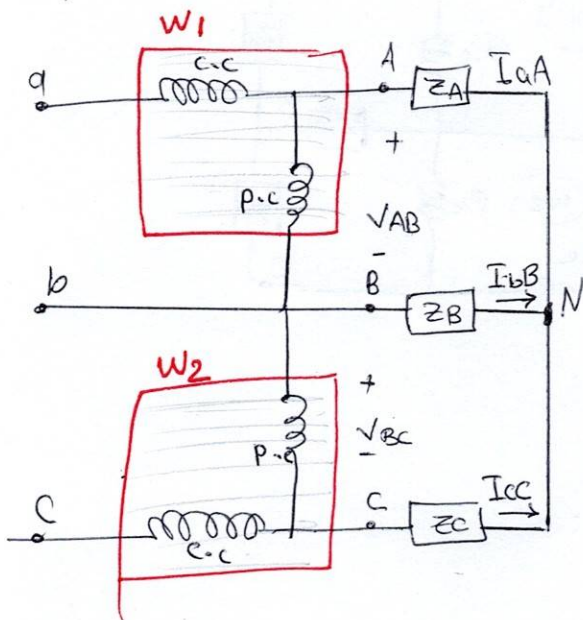
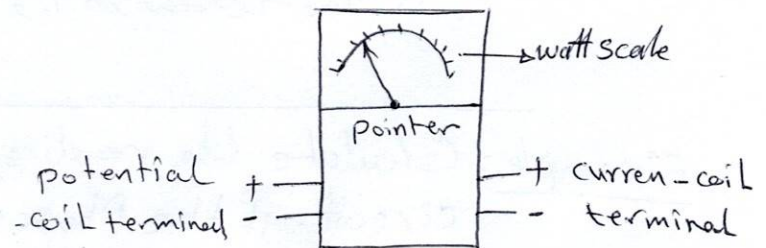


= Wattmeter Reading =

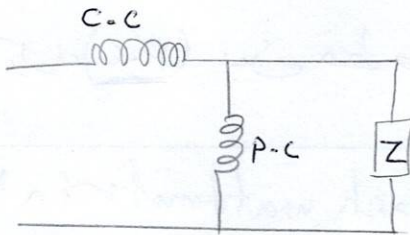

$$W_1 = |V_{AB}| |I_{aA}| \cos(\theta\phi + 30^\circ)$$

$$W_2 = |V_{CB}| |I_{cC}| \cos(\theta\phi - 30^\circ)$$

$$\Rightarrow |V_{AB}| \Rightarrow V_L = |V_{CB}|$$

$$\Rightarrow |I_{aA}| \Rightarrow I_L = |I_{cC}|$$

$$\begin{aligned} W_1 &= V_L I_L \cos(\theta\phi + 30^\circ) \\ W_2 &= V_L I_L \cos(\theta\phi - 30^\circ) \end{aligned}$$


$$\theta = \tan^{-1} \left[\frac{\sqrt{3} (W_2 - W_1)}{W_2 + W_1} \right]$$

(2)

- ملاحظة:
- ١- يكون (c.c) على امتداد الخط . وتأخذ من قيمة (I_{line}) .
- ٢- يكون (p.c) بين خط وخط . وتأخذ من قيمة (V_{line}) .

Example: Calculate the reading of each wattmeter in the circuit. if the Phase voltage at the load is $(120) V$.

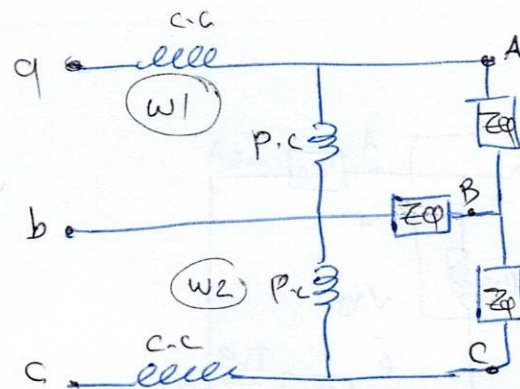- a) $Z_{\phi} = 8 + j6 \Omega$
 b) $Z_{\phi} = 8 - j6 \Omega$
 c) $Z_{\phi} = 5 + j5\sqrt{3} \Omega$
 d) $Z_{\phi} = 10 \angle -75^\circ \Omega$



Solution :

a) $Z_{\phi} = 8 + j6 \Omega$, $V_{\phi} = 120 V$.

$$Z_{\phi} = r \angle \theta_{\phi}$$

$$Z_{\phi} = 10 \angle 36.87^\circ$$

$$\therefore \theta_{\phi} = 36.87^\circ$$

الربط $\rightarrow V_L = \sqrt{3} V_{\phi}$, $I_L = I_{\phi}$

$$V_L = 120\sqrt{3}$$

$$I_L = I_{\phi} = \frac{V_{\phi}}{Z_{\phi}} = \frac{120 \angle 0^\circ}{10 \angle 36.87^\circ} = 12 \angle -36.87^\circ A$$

$$W_1 = |V_L| |I_L| \cos(\theta_{\phi} + 30^\circ) = (120\sqrt{3})(12) \cos(36.87^\circ + 30^\circ)$$

$$W_1 = 979.75 W$$

$$W_2 = |V_L| |I_L| \cos(\theta_{\phi} - 30^\circ) = 2476.25 W$$

$$P_T = W_1 + W_2 = 979.75 + 2476.25 = 3456 W$$

(3)

$$b) Z\phi = 10 \angle -36.87$$

$$I_L = I\phi = \frac{V\phi}{Z\phi} = \frac{120 \angle 0}{10 \angle -36.87} = 12 \angle 36.87 \text{ A}$$

$$W_1 = (120 \sqrt{3})(12) \cos(-36.87 + 30) = 2476.25 \text{ W}$$

$$W_2 = (120 \sqrt{3})(12) \cos(-36.87 - 30) = 979.75 \text{ W}$$

$$P_T = W_1 + W_2 = 3456 \text{ W}$$

$$c) Z\phi = 5 + j5\sqrt{3}$$

$$Z\phi = 10 \angle 60$$

$$W_1 = (120 \sqrt{3})(12) \cos(\overbrace{60}^{90} + 30) \rightarrow \cos 90 = 0$$

$$W_1 = 0$$

$$W_2 = (120 \sqrt{3})(12) \cos(60 - 30) = 2160 \text{ W}$$

$$d) Z\phi = 10 \angle -75$$

$$W_1 = 1763 \text{ W}$$

$$W_2 = -645.53 \text{ W}$$

$$P_T = 1118.1 \text{ W}$$

ملاحظة / للتأكد من الحل بالسبب لرفع (a)

$$P_T = 3(I^2) \times R \\ = 3(12)^2 \times 8 = 3456 \text{ W}$$

وكذلك بالسبب لبقية الفروع،


(4)

Ex: the wattmeters have a data, Find $Z\phi$.

$$W_1 = 40823.09 \text{ W}$$

$$W_2 = 103176.91 \text{ W}$$

$$V_L = 2400 \sqrt{3} \text{ V}$$

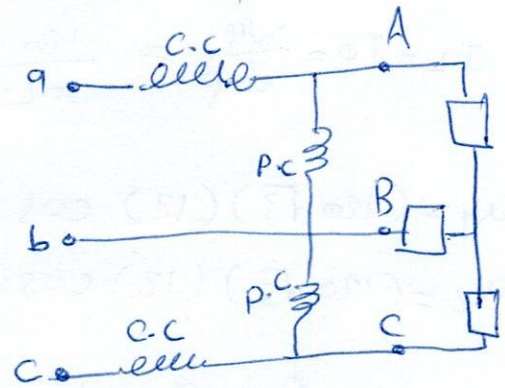

Solution

$$\theta_\phi = \tan^{-1} \left[\frac{\sqrt{3} (W_2 - W_1)}{W_2 + W_1} \right]$$

$$\boxed{\theta_\phi = 36.87^\circ}$$

$$W_1 = V_L I_L \cos (\theta_\phi + 30^\circ)$$

$$40823.09 = (2400\sqrt{3}) (I_L) \cos (36.87^\circ + 30^\circ)$$

$$I_L = 25 \text{ A}$$

$$Z_\phi = \frac{V_\phi}{I_\phi}$$

$$Y \Rightarrow I_\phi = I_L, V_L = \sqrt{3} V_\phi$$

$$\therefore \boxed{I_\phi = 25 = I_L}$$

$$V_\phi = \frac{V_L}{\sqrt{3}} = \frac{2400\sqrt{3}}{\sqrt{3}} = 2400 \text{ V}$$

$$\therefore Z_\phi = \frac{2400}{25} = 96 \Omega$$


$$\boxed{Z_\phi = 96 \angle 36.87^\circ \Omega} \text{ يجب وضع الراديان}$$

(5)

Ex: A balanced 3- ϕ load shown in fig. below, is fed from a balanced positive sequence, 3 ϕ , Y-connected Source with p.f. of (0.96) lagging. The line-to-neutral voltage of the Source is 7200 V. Find:-

a) wattmeter reading in watt.

b) Phase impedance. Z_{ϕ} .

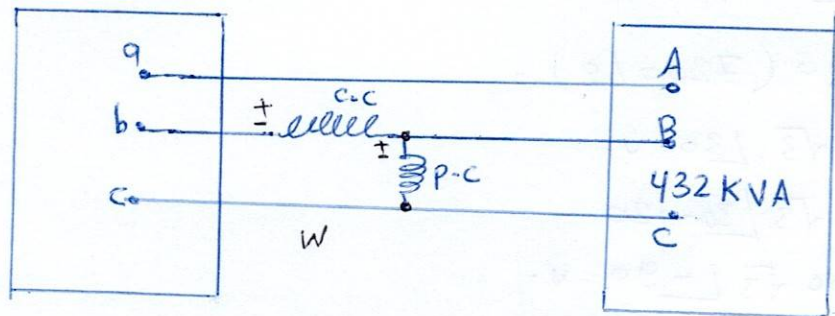

Solution :

* في البداية نحدد مكان (Wattmeter)
لكي نعرف اي تيار واي فولتية
نحتاج للقرارة.

a)

$$p.f = 0.96 = \cos \theta$$

$$\theta = \cos^{-1}(0.96) = 16.26^\circ$$

$$S = 432 \text{ KVA} \rightarrow \text{يجب أن تحول إلى قيمة دارة}$$

$$S = \frac{432}{3} \cos \theta + j \frac{432}{3} \sin \theta$$

$$S = 144 \times 0.96 + j 144 \sin (16.26^\circ)$$

$$S = 138.24 + j 40.32 \text{ KVA}$$

$$\text{also: } S = V_{\phi} \times I_{\phi}^*$$

$$I_{\phi} = I_{\phi A} = I_L$$

$$I_{\phi A}^* = \frac{S}{V_{\phi}} = \frac{(138.24 + j 40.32) \times 10^3}{7200} = \frac{(144 \angle 16.26^\circ) 10^3}{7200 \angle 0} = 20 \angle 16.26^\circ \text{ A}$$

$$I_{\phi A} = 20 \angle -16.26^\circ \text{ A}$$

⑥

$$\cancel{I_{bB}} = 20 \angle -16.26 - 120 = 20 \angle -136.26^\circ \text{ A}$$

$$\begin{cases} V_{AN} = V_\phi = 7200 \angle 0^\circ \text{ V.} \\ V_{BN} = 7200 \angle 0 - 120^\circ \text{ V.} \\ V_{CN} = 7200 \angle +120^\circ \text{ V.} \end{cases}$$

$$V_{AB} = \sqrt{3} \angle 30^\circ V_{AN}$$

$$V_{AB} = \sqrt{3} \angle 30^\circ (7200 \angle 0^\circ)$$

$$\begin{cases} V_{AB} = 7200 \sqrt{3} \angle 30^\circ \text{ V.} \\ V_{BC} = 7200 \sqrt{3} \angle 30 - 120^\circ \\ V_{BC} = 7200 \sqrt{3} \angle -90^\circ \text{ V.} \end{cases}$$

$$W = |V_L| |I_L| \cos(\theta_\phi + 30^\circ)$$

$$W = |V_{BC}| |I_{bB}| \cos(16.26^\circ + 30^\circ)$$

$$W = (7200 \sqrt{3})(20) \cos(46.26^\circ)$$


$$W = 172442.5 \text{ W}$$

⑥ Z_ϕ

$$Z_\phi = \frac{V_\phi}{I_\phi} = \frac{V_{AN}}{I_{aA}} = \frac{7200 \angle 0^\circ}{20 \angle -16.26^\circ} =$$

$$Z_\phi = 360 \angle 16.26^\circ \Omega \approx 1\phi$$

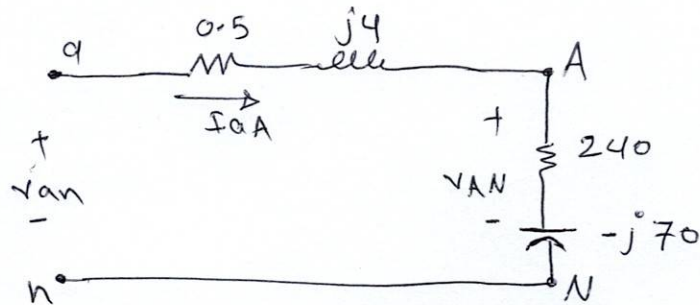Ex: The magnitude of Line voltage at Y-load is 6600 V.
 the $Z_A = (240 - j70) \Omega/\phi$. $Z_L = (0.5 + j4) \Omega/\phi$. Find:-
 ① magnitude of line current.



Sol: Y-connected $\Rightarrow \begin{cases} V_L = \sqrt{3} V_\phi \\ I_L = I_\phi \end{cases} = I_{aA}$

$$V_L = 6600$$

$$V_\phi = \frac{6600}{\sqrt{3}} \text{ V} = V_{AN}$$

$$I_{aA} = \frac{V_{AN}}{Z_A} = \frac{6600/\sqrt{3}}{240 - j70} = 15.24 \angle 16.26^\circ \text{ A}$$

$$|I_{aA}| = |I_L| = 15.24 \text{ A}$$

② Magnitude of line voltage at the source.

$$\begin{aligned} V_{an} &= I_{aA} \times (Z_L + Z_A) \\ &= (15.24 \angle 16.26^\circ) \times [(0.5 + j4) + (240 - j70)] \\ &= 3801.24 \angle 0.91^\circ \text{ V} \end{aligned}$$

$$V_{ab} = V_L \rightarrow \text{at source}$$

$$Y \rightarrow V_L = \sqrt{3} V_\phi$$

$$|V_{ab}| = \sqrt{3} |V_{an}| = \sqrt{3} (3801.24) = 6583.94 \text{ V}$$