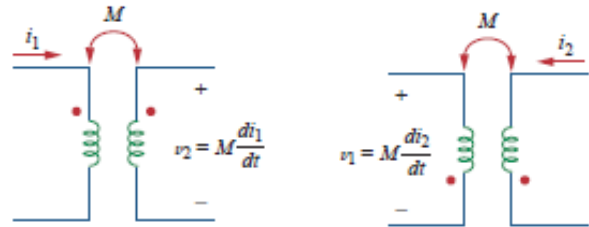




Mutual Inductance

Mutual inductance is the ability of one inductor to induce a voltage across a neighboring inductor, measured in henrys (H).

$$L = L_1 + L_2 + 2M \quad (\text{Series-aiding connection})$$



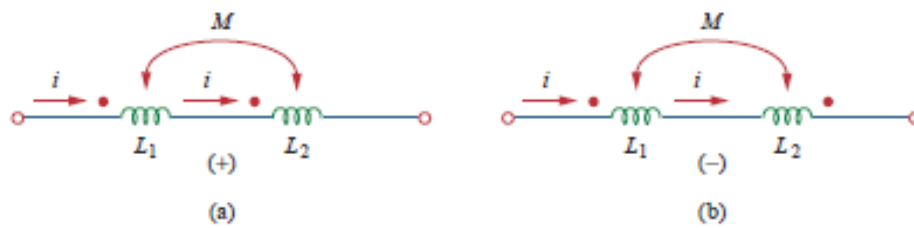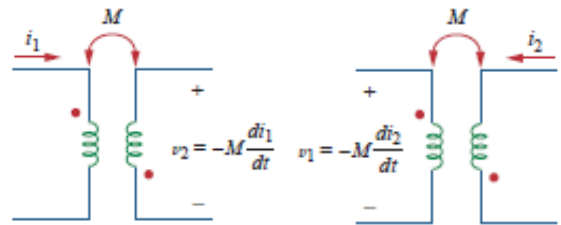
$$L = L_1 + L_2 - 2M \quad (\text{Series-opposing connection})$$



Figure

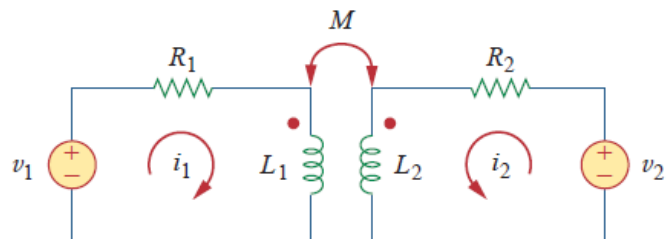Dot convention for coils in series; the sign indicates the polarity of the mutual voltage:
(a) series-aiding connection, (b) series-opposing connection



Figure


Time-domain analysis of a circuit containing coupled coils.

KVL to coil 1 gives

$$v_1 = i_1 R_1 + L_1 \frac{di_1}{dt} + M \frac{di_2}{dt}$$

For coil 2, KVL gives
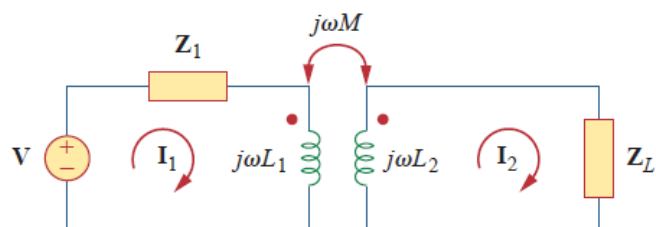
$$v_2 = i_2 R_2 + L_2 \frac{di_2}{dt} + M \frac{di_1}{dt}$$



Figure

Frequency-domain analysis of a circuit containing coupled coils.

in the frequency domain. Applying KVL to coil 1, we get


$$\mathbf{V} = (\mathbf{Z}_1 + j\omega L_1)\mathbf{I}_1 - j\omega M\mathbf{I}_2$$

For coil 2, KVL yields

$$0 = -j\omega M\mathbf{I}_1 + (\mathbf{Z}_L + j\omega L_2)\mathbf{I}_2$$

Calculate the phasor currents $\mathbf{I}_1$ and $\mathbf{I}_2$ in the circuit of Fig. 13.9.

Example

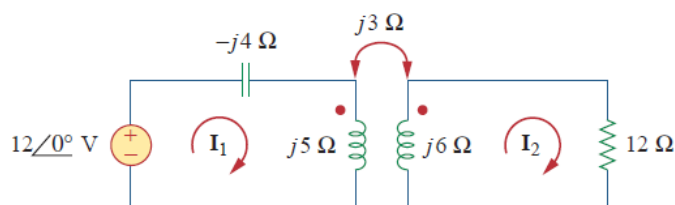

Solution:

For coil 1, KVL gives

$$-12 + (-j4 + j5)\mathbf{I}_1 - j3\mathbf{I}_2 = 0$$

or

$$j\mathbf{I}_1 - j3\mathbf{I}_2 = 12$$

For coil 2, KVL gives.

$$-j3\mathbf{I}_1 + (12 + j6)\mathbf{I}_2 = 0$$

or

$$\mathbf{I}_1 = \frac{(12 + j6)\mathbf{I}_2}{j3} = (2 - j4)\mathbf{I}_2$$

Substituting this in

$$(j2 + 4 - j3)\mathbf{I}_2 = (4 - j)\mathbf{I}_2 = 12$$

or


$$\mathbf{I}_2 = \frac{12}{4 - j} = 2.91\angle 14.04^\circ \text{ A}$$

From Eqs. (13.1.2) and (13.1.3),

$$\begin{aligned}\mathbf{I}_1 &= (2 - j4)\mathbf{I}_2 = (4.472\angle -63.43^\circ)(2.91\angle 14.04^\circ) \\ &= 13.01\angle -49.39^\circ \text{ A}\end{aligned}$$

Practice Problem

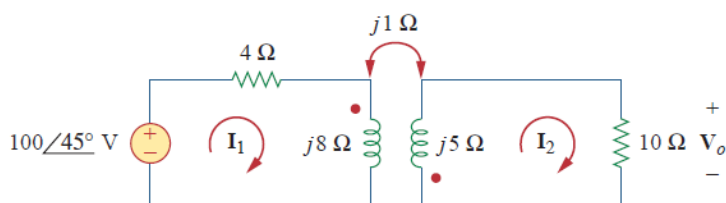Determine the voltage $\mathbf{V}_o$ in the circuit



Energy in a Coupled Circuit

$$w = \frac{1}{2}L_1 i_1^2 + \frac{1}{2}L_2 i_2^2 \pm M i_1 i_2$$

Coefficient of coupling k

$$k = \frac{M}{\sqrt{L_1 L_2}}$$

The coupling coefficient k is a measure of the magnetic coupling between two coils; $0 \leq k \leq 1$


$k = 1$ perfectly coupled

$k < 0.5$, loosely coupled

$k > 0.5$, tightly coupled

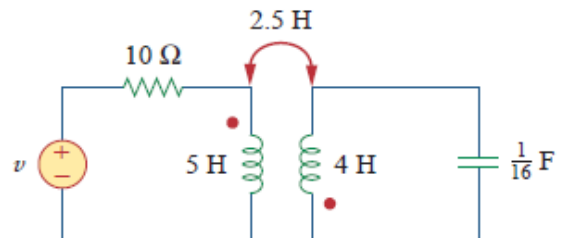Example

Consider the circuit in Fig. Determine the coupling coefficient. Calculate the energy stored in the coupled inductors at time $t = 1$ s if $v = 60 \cos(4t + 30^\circ)$ V.



Solution:

The coupling coefficient is

$$k = \frac{M}{\sqrt{L_1 L_2}} = \frac{2.5}{\sqrt{20}} = 0.56$$

indicating that the inductors are tightly coupled. To find the energy stored, we need to calculate the current. To find the current, we need to obtain the frequency-domain equivalent of the circuit.


$$60 \cos(4t + 30^\circ) \Rightarrow 60 \angle 30^\circ, \quad \omega = 4 \text{ rad/s}$$

$$5 \text{ H} \Rightarrow j\omega L_1 = j20 \Omega$$

$$2.5 \text{ H} \Rightarrow j\omega M = j10 \Omega$$

$$4 \text{ H} \Rightarrow j\omega L_2 = j16 \Omega$$
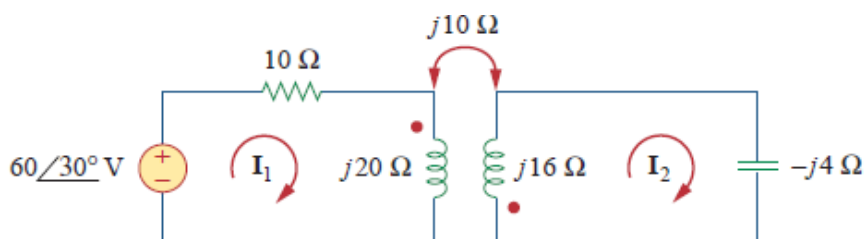
$$\frac{1}{16} \text{ F} \Rightarrow \frac{1}{j\omega C} = -j4 \Omega$$



We now apply mesh analysis. For mesh 1

$$(10 + j20)\mathbf{I}_1 + j10\mathbf{I}_2 = 60\angle 30^\circ$$

For mesh 2,

$$j10\mathbf{I}_1 + (j16 - j4)\mathbf{I}_2 = 0$$

or

$$\mathbf{I}_1 = -1.2\mathbf{I}_2$$

$$\mathbf{I}_2(-12 - j14) = 60\angle 30^\circ \Rightarrow \mathbf{I}_2 = 3.254\angle \underline{\hspace{1cm}} \text{ A}$$

and

$$\mathbf{I}_1 = -1.2\mathbf{I}_2 = 3.905\angle -19.4^\circ \text{ A}$$

In the time-domain,

$$i_1 = 3.905 \cos(4t - 19.4^\circ), \quad i_2 = 3.254 \cos(4t + 160.6^\circ)$$

At time $t = 1 \text{ s}$, $4t = 4 \text{ rad} = 229.2^\circ$, and

$$i_1 = 3.905 \cos(229.2^\circ - 19.4^\circ) = -3.389 \text{ A}$$

$$i_2 = 3.254 \cos(229.2^\circ + 160.6^\circ) = 2.824 \text{ A}$$


The total energy stored in the coupled inductors is

$$w = \frac{1}{2}L_1 i_1^2 + \frac{1}{2}L_2 i_2^2 + M i_1 i_2$$

$$= \frac{1}{2}(5)(-3.389)^2 + \frac{1}{2}(4)(2.824)^2 + 2.5(-3.389)(2.824) = 20.73 \text{ J}$$

For the circuit in Fig. determine the coupling coefficient and the energy stored in the coupled inductors at $t = 1.5 \text{ s}$.

Practice Problem

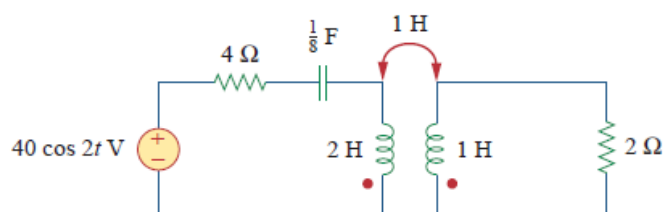

Linear Transformers

A transformer is a magnetic device that takes advantage of the phenomenon of mutual inductance. A transformer is generally a four-terminal device comprising two (or more) magnetically coupled coils. It is used in changing the current, voltage, or impedance level in a circuit.

A linear (or loosely coupled) transformer has its coils wound on a magnetically linear material. It can be replaced by an equivalent T or π network for the purposes of analysis.


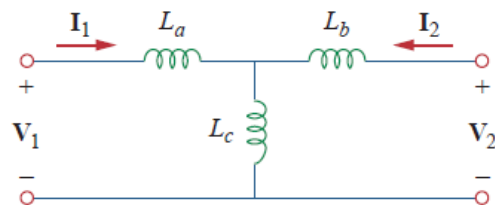
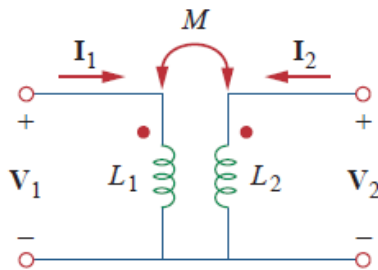


Figure
An equivalent T circuit.

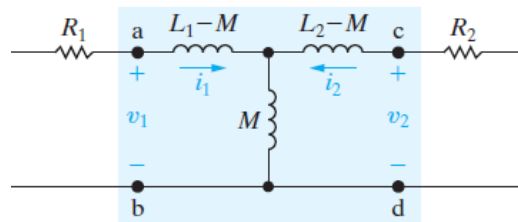the equivalent circuit of a
linear transformer




$$L_a = L_1 - M, \quad L_b = L_2 - M, \quad L_c = M$$

$$x_L = j\omega L = j2\pi f c$$



$$x_C = \frac{1}{j\omega c} = -\frac{j}{2\pi f c}$$

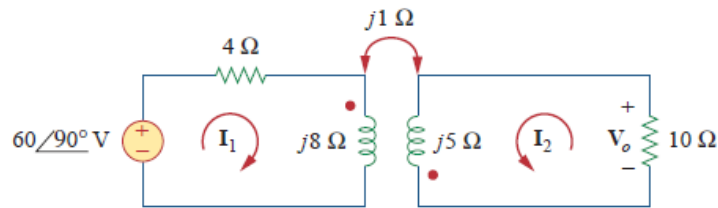Example Solve for $\mathbf{I}_1$, $\mathbf{I}_2$, and $\mathbf{V}_o$ using the T-equivalent circuit for the linear transformer.



$$L_a = L_1 - (-M) = 8 + 1 = 9 \text{ H}$$

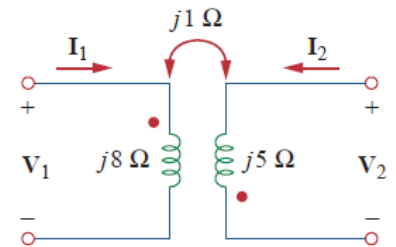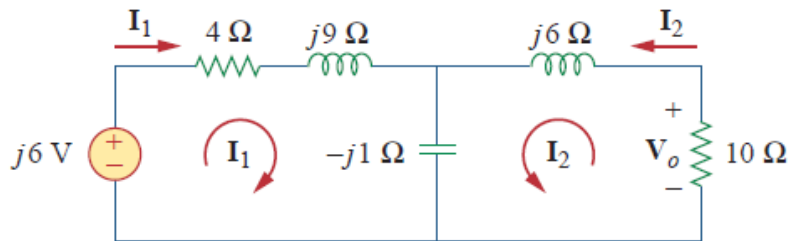
$$L_b = L_2 - (-M) = 5 + 1 = 6 \text{ H}, \quad L_c = -M = -1 \text{ H}$$



$$j6 = \mathbf{I}_1(4 + j9 - j1) + \mathbf{I}_2(-j1)$$

$$0 = \mathbf{I}_1(-j1) + \mathbf{I}_2(10 + j6 - j1)$$
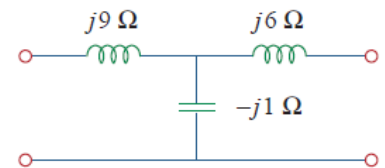
$$\mathbf{I}_1 = \frac{(10 + j5)}{j} \mathbf{I}_2 = (5 - j10) \mathbf{I}_2$$



$$j6 = (4 + j8)(5 - j10) \mathbf{I}_2 - j \mathbf{I}_2 = (100 - j) \mathbf{I}_2 \approx 100 \mathbf{I}_2$$

Since 100 is very large compared with 1, the imaginary part of $(100 - j)$ can be ignored so that $100 - j \approx 100$. Hence,


$$\mathbf{I}_2 = \frac{j6}{100} = j0.06 = 0.06 \angle 90^\circ \text{ A}$$

$$\mathbf{I}_1 = (5 - j10)j0.06 = 0.6 + j0.3 \text{ A}$$

and

$$\mathbf{V}_o = -10 \mathbf{I}_2 = -j0.6 = 0.6 \angle -90^\circ \text{ V}$$


Q/

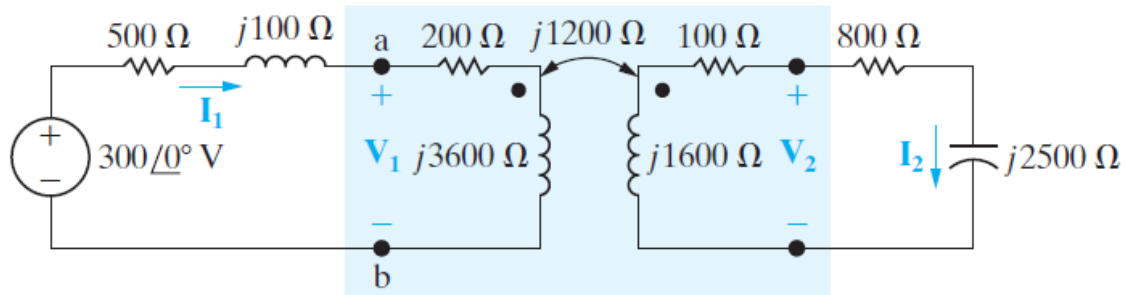


- Use the T-equivalent circuit for the magnetically coupled coils shown in Fig. C.6 to find the phasor currents I_1 and I_2 . The source frequency is 400 rad/s .
- Repeat (a), but with the polarity dot on the secondary winding moved to the lower terminal.

Mutual inductance examples

Q1/ For the circuit in Fig., find V_o .

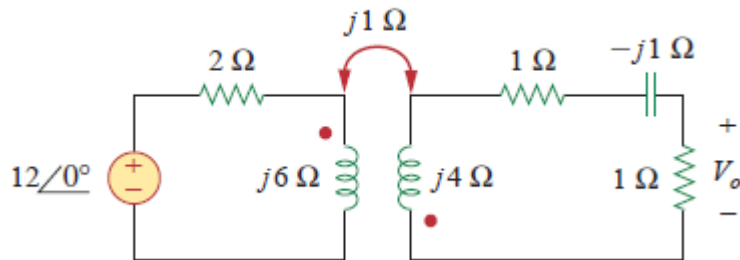

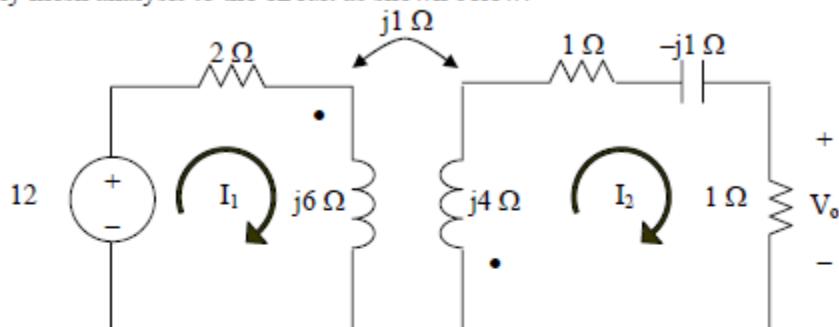We apply mesh analysis to the circuit as shown below.



For mesh 1,

$$12 = I_1(2 + j6) + jI_2 \quad (1)$$

For mesh 2,

$$0 = jI_1 + (2 - j1 + j4)I_2$$

or

$$0 = jI_1 + (2 + j3)I_2 \quad (2)$$

In matrix form,

$$\begin{bmatrix} 12 \\ 0 \end{bmatrix} = \begin{bmatrix} 2 + j6 & j \\ j & 2 + j3 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$I_2 = -0.4381 + j0.3164$$

$$V_o = I_2 \times 1 = \underline{540.5 \angle 144.16^\circ \text{ mV}}$$

$$\Delta = \begin{vmatrix} 2 + j6 & j \\ j & 2 + j3 \end{vmatrix} = 4 + j2 + j6 - 18 + 1 = -13 + j18$$

$$\Delta_1 = \begin{vmatrix} 12 & j \\ 0 & 2 + j3 \end{vmatrix} = 24 + j36$$

$$\Delta_2 = \begin{vmatrix} 2+j6 & 12 \\ j & 0 \end{vmatrix} = 0 - j12 = -j12$$

$$I_1 = \frac{\Delta_1}{\Delta} = \frac{24 + j36}{-13 + j18} = \frac{43.26 \angle 56.31}{22.2 \angle -54.16} = 1.94 \angle 110.47$$

$$I_2 = \frac{\Delta_2}{\Delta} = \frac{-j12}{-13 + j18} = \frac{(-j12) * (-13 - j18)}{(-13 + j18) * (-13 - j18)} = \frac{j156 - 216}{493} =$$


$$= -0.438 + j0.316$$

الحل اعلاه هو بطريقة المصفوفة يمكنك اتباعها.

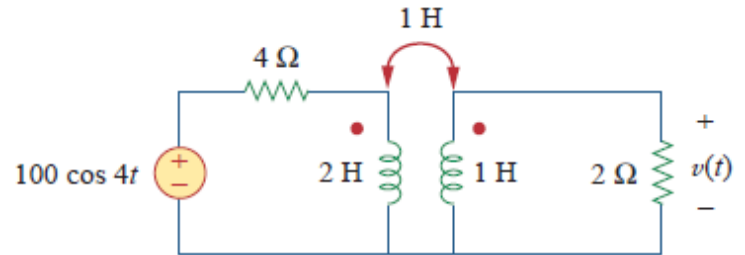
Q2/Find $v(t)$ for the circuit in Fig.

$$2H \longrightarrow j\omega L = j4 \times 2 = j8$$

$$1H \longrightarrow j\omega L = j4 \times 1 = j4$$



Consider the circuit below.

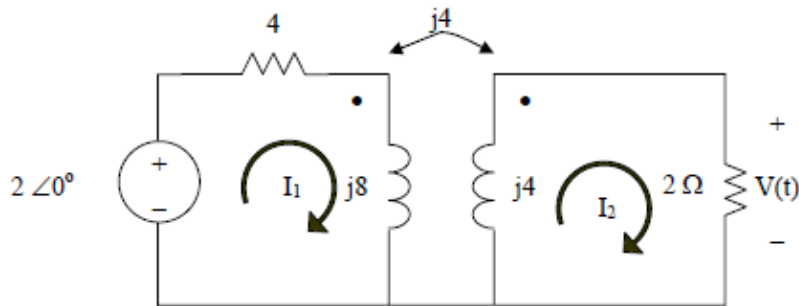

$$2 = (4 + j8)I_1 - j4I_2 \quad (1)$$

$$0 = -j4I_1 + (2 + j4)I_2 \quad (2)$$

In matrix form, these equations become

$$\begin{bmatrix} 2 \\ 0 \end{bmatrix} = \begin{bmatrix} 4 + j8 & -j4 \\ -j4 & 2 + j4 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

Solving this leads to


$$I_2 = 0.2353 - j0.0588$$

$$V = 2I_2 = 0.4851 \angle -14.04^\circ$$

Thus,


$$v(t) = 0.4851 \cos(4t - 14.04^\circ) \text{ V}$$

Q3/Find V_x for the circuit in Fig.

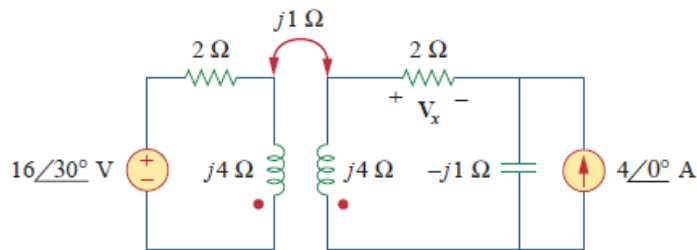

- عن طريق تحويل مصدر التيار الى مصدر فولتية
- افرض اتجاه التيار كما ترغب

Consider the circuit below.

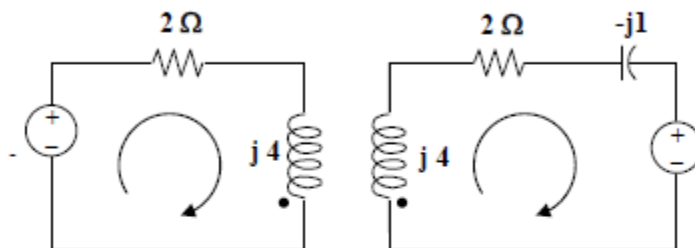

For loop 1,

$$8\angle 30^\circ = (2 + j4)I_1 - jI_2 \quad (1)$$

For loop 2,

$$((j4 + 2 - j)I_2 - jI_1 + (-j2)) = 0$$

$$\text{or } I_1 = (3 - j2)I_2 - 2 \quad (2)$$

Substituting (2) into (1),

$$8\angle 30^\circ + (2 + j4)2 = (14 + j7)I_2$$

$$I_2 = (10.928 + j12)/(14 + j7) = 1.037\angle 21.12^\circ$$

$$V_x = 2I_2 = \underline{2.074\angle 21.12^\circ}$$

يمكنك حل المعادلات بطريقة التعويض او بطريقة المصفوفة كما في السؤال الاول

Q4/ If $M = 0.2$ H and $v_s = 120 \cos 10t$ V in the circuit of Fig. , find i_1 and i_2 . Calculate the energy stored in the coupled coils at $t = 15$ ms.

$$\omega = 10$$



$$0.5 \text{ H converts to } j\omega L_1 = j5 \text{ ohms}$$

$$1 \text{ H converts to } j\omega L_2 = j10 \text{ ohms}$$

$$0.2 \text{ H converts to } j\omega M = j2 \text{ ohms}$$

$$25 \text{ mF converts to } 1/(j\omega C) = 1/(10 \times 25 \times 10^{-3}) = -j4 \text{ ohms}$$

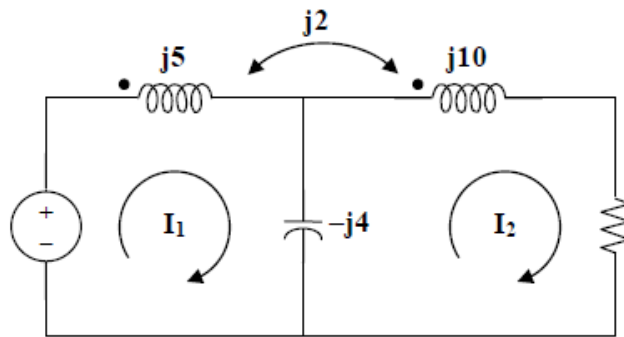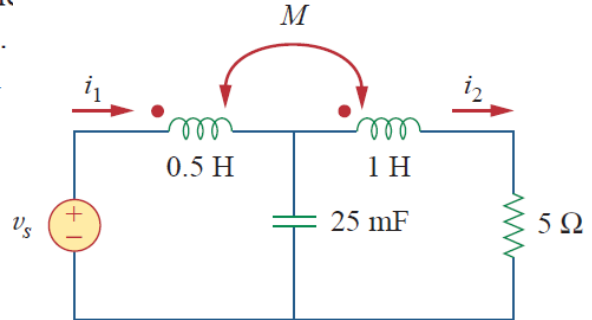The frequency-domain equivalent circuit is shown below.



For mesh 1, $12 = (j5 - j4)I_1 + j2I_2 - (-j4)I_2$

$$-j12 = I_1 + 6I_2 \quad (1)$$

For mesh 2, $0 = (5 + j10)I_2 + j2I_1 - (-j4)I_1$

$$0 = (5 + j10)I_2 + j6I_1 \quad (2)$$

From (1), $I_1 = -j12 - 6I_2$

Substituting this into (2) produces,

$$I_2 = 72/(-5 + j26) = 2.7194 \angle -100.89^\circ$$

$$I_1 = -j12 - 6I_2 = -j12 - 163.17 \angle -100.89^\circ = 5.068 \angle 52.54^\circ$$

Hence,

$$i_1 = \underline{5.068 \cos(10t + 52.54^\circ) \text{ A}}, \quad i_2 = \underline{2.719 \cos(10t - 100.89^\circ) \text{ A}}$$


At $t = 15$ ms, $10t = 10 \times 15 \times 10^{-3} = 0.15 \text{ rad} = 8.59^\circ$

$$i_1 = 5.068 \cos(61.13^\circ) = 2.446$$

$$i_2 = 2.719 \cos(-92.3^\circ) = -0.1089$$

$$w = 0.5(5)(2.446)^2 + 0.5(1)(-0.1089)^2 - (0.2)(2.446)(-0.1089) = \underline{15.02 \text{ J}}$$

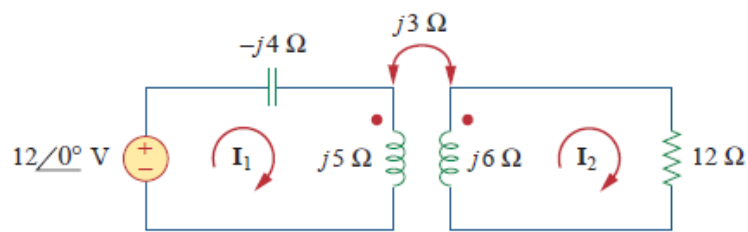
Q5/ Calculate the phasor currents I_1 and I_2 in the circuit using T-equivalent cct for linear transformer.



Answer: $13\angle 49.4^\circ \text{ A}$,


$2.91\angle 14.04^\circ \text{ A}$.

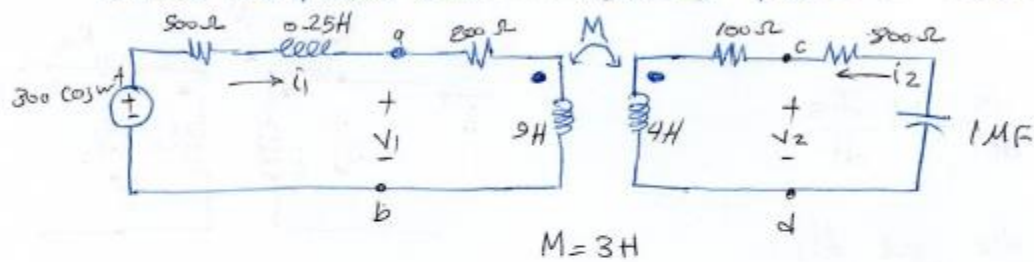Ex: Use the T-equ. ckt. for the magnitally coupled coils shown to find the phaser current (I_1, I_2), $\omega = 400 \text{ rad/s}$.



Sol:
T-equ. ckt. needs
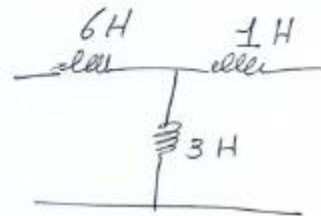
$$\left. \begin{aligned} L_1 - M &= 9 - 3 = 6 \text{ H} \\ L_2 - M &= 4 - 3 = 1 \text{ H} \\ M &= 3 \text{ H} \end{aligned} \right\}$$



So we have to Find X_L, X_C


$$X_{L1} = j\omega L_1 = j(400)(6) = j2400 \Omega$$

$$X_{L2} = j\omega L_2 = j(400)(1) = j400 \Omega$$

$$X_{L3} = j\omega M = j(400)(3) = j1200 \Omega$$

$$X_{L4} = j\omega(0.25 \text{ H}) = j(400)(0.25) = j100 \Omega$$
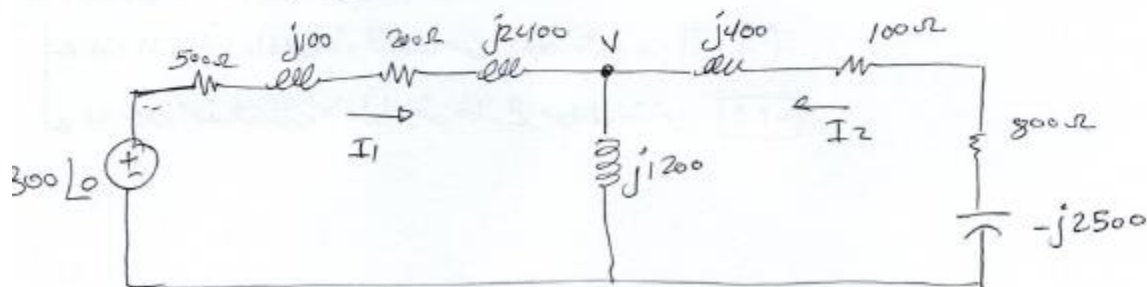
$$X_C = \frac{j}{\omega C} = j \frac{1}{(400)(10^{-6})} = j2500 \Omega$$



To Find I_1, I_2 , we will use Nodal method

$$\frac{V-300}{700+j2500} + \frac{V}{j1200} + \frac{V}{900-j2100} = 0$$

$$V = 136 - j8 = 136.24 \angle -3.37^\circ \text{ V}$$

$$\text{then } I_1 = \frac{300 - (136 - j8)}{700 + j2500} = 63.25 \angle -71.57^\circ \text{ mA}$$

$$I_2 = \frac{136 - j8}{900 - j2100} = 59.63 \angle 63.43^\circ \text{ mA}$$