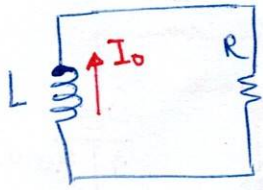


①


Leet. -4-

« A general Solution for step and Natural Response »




$$L \frac{di}{dt} + Ri = 0$$

$$\frac{di}{dt} + \frac{R}{L} i = 0$$

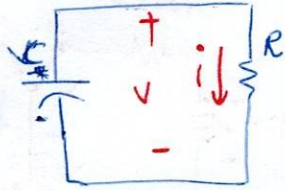


$$C \frac{dv}{dt} + \frac{v}{R} = 0$$

$$\frac{dv}{dt} + \frac{1}{RC} v = 0$$

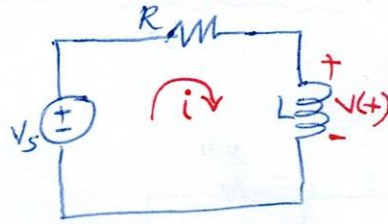

$$V_s = Ri + L \frac{di}{dt}$$
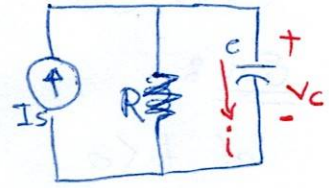
$$\frac{di}{dt} + \frac{R}{L} i = \frac{V_s}{L}$$



$$I_s = \frac{v}{R} + C \frac{dv}{dt}$$

$$\frac{dv}{dt} + \frac{1}{RC} v = \frac{I_s}{C}$$

➤ in general :-

$$\frac{dx}{dt} + \frac{1}{\tau} x = k$$

$$\frac{dx}{dt} = -\frac{1}{\tau} x + k$$

$$\frac{dx}{dt} = -\left(\frac{x}{\tau} - k\right)$$

$$\frac{dx}{dt} = -\left(\frac{x - k\tau}{\tau}\right)$$

, when $k\tau = x_f$

$$\frac{dx}{dt} = -\left(\frac{x - x_f}{\tau}\right)$$

$$\int_{x_0}^{x(t)} \frac{dx}{(x - x_f)} = -\int_{t_0}^t \frac{1}{\tau} dt \quad \left. \vphantom{\int_{x_0}^{x(t)}} \right\} \text{by integral two terminals}$$

$$x(t) = x_f + [x(t_0) - x_f] e^{-(t-t_0)/\tau}$$

General equation


①

Ex: the switch in the ckt has been in position a for along time. At $t=0$, the switch is moved to position b. Find


a) initial value of V_C ?

Sol s:-

at $t < 0$

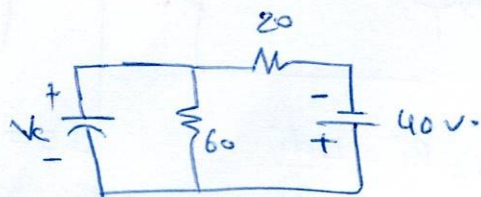

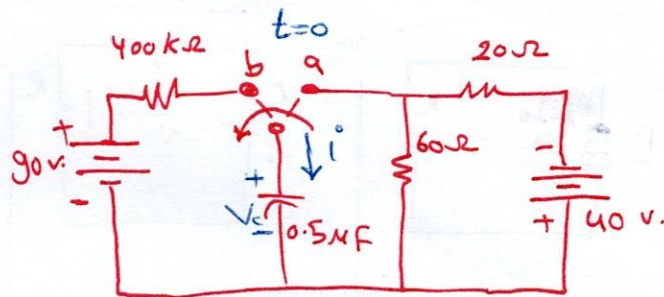
$$V_C(0) = V_0 = -40 \times \frac{60}{60+20} = -30 \text{ V.}$$



b) Final value of V_C ?

at $t \geq 0$

$$V_f = V_s = 90 \text{ V.}$$

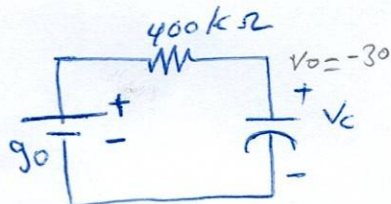

c) expression of $V_C(t)$ at $t \geq 0$?

$$\tau = RC = 400 \times 10^3 \times 0.5 \times 10^{-6} = 0.2 \text{ s}$$

$$V_C(t) = V_f + [V_0 - V_f] e^{-(t-t_0)/\tau}$$

$$V_C(t) = 90 + (-30 - 90) e^{-(t-0)/0.2}$$

$$V_C(t) = 90 - 120 e^{-5t} \text{ V.}, t \geq 0$$

d) find $i(t)$

$$i(t) = C \frac{dV_C(t)}{dt} = 0.5 \times 10^{-6} \left(\frac{d}{dt} (90 - 120 e^{-5t}) \right) = (0.5 \times 10^{-6}) (600 e^{-5t}) = 300 e^{-5t} \mu\text{A}$$

e) How long after the δ in position b does $V_C = 0$?

$$0 = 90 - 120 e^{-5t}$$

$$90 = 120 e^{-5t} \Rightarrow t = 57.54 \text{ ms}$$

(3)

Ex: Find $v(t)$, $i(t)$?

at $t < 0$

$$v_0 = 0$$

at $t \geq 0$

$$\tau = RC = 50 \cdot 10^3 \times 0.1 \times 10^{-6} \\ = 5 \text{ ms}$$

$$V_f = 150 \text{ V}$$

$$x(t) = x_f + (x_0 - x_f) e^{-t/\tau}$$

$$v(t) = 150 + (0 - 150) e^{-t/0.005}$$


$$\boxed{v(t) = 150 - 150 e^{-200t} \text{ V}}$$

$$i(t) = i_c(t) = C \frac{dv(t)}{dt} \\ = C \cdot \frac{d(150 - 150 e^{-200t})}{dt} \\ = 0.1 \times 10^{-6} (-150 \times -200 e^{-200t})$$

$$\boxed{i(t) = 3 e^{-200t} \text{ mA}}$$



$$V_{30k\Omega} = i(t) \times R_{30}$$
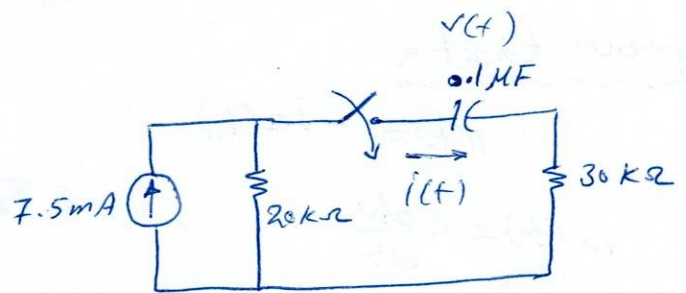
$$= 3 e^{-200t} \times 10^{-3} \times 30 \times 10^3 = 90 e^{-200t}$$



قوي المصدر، المقاومة، المكثف، الجهد
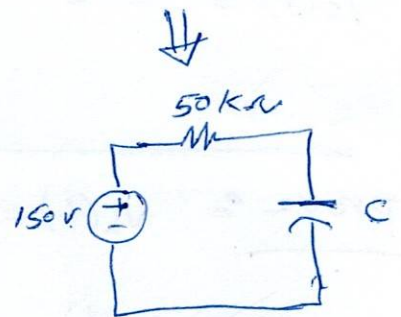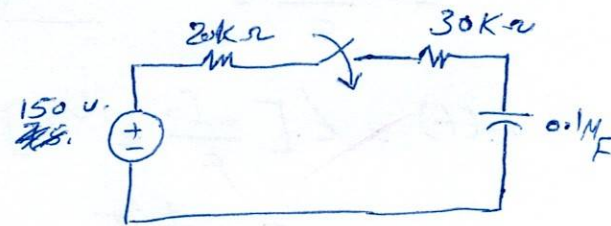
$$7.5 \cdot 10^{-3} \times 20 \cdot 10^3 = 150 \text{ V}$$



(4)

prove that:

$$i(t) = -i_c(t)$$

$$i_c(t) = C \frac{dv}{dt}, \quad v = R \cdot I_0 e^{-t/\tau}, \quad \tau = R \cdot C$$

$$\frac{dv}{dt} = R \cdot I_0 \left(-\frac{1}{\tau}\right) e^{-t/\tau}$$

$$= R \cdot I_0 \left(-\frac{1}{RC}\right) e^{-t/\tau}$$

$$= -\frac{I_0}{C} e^{-t/\tau}$$

sub in $i_c(t)$ equation

$$i_c(t) = C \cdot \left[-\frac{I_0}{C} e^{-t/\tau}\right]$$

$$i_c(t) = -I_0 e^{-t/\tau} = -i(t)$$

prove: $v_L(t) = -v(t)$

$$v_L(t) = L \frac{di}{dt}, \quad i = \frac{V_0}{R} e^{-t/\tau}, \quad \tau = \frac{L}{R}$$

$$\frac{di}{dt} = \frac{V_0}{R} \cdot \left(-\frac{1}{\tau}\right) e^{-t/\tau}$$

$$= -\frac{V_0}{L} e^{-t/\tau} \quad \text{sub in eq. of } v_L(t)$$

$$v_L(t) = L \left[-\frac{V_0}{L} e^{-t/\tau}\right]$$

$$v_L(t) = -V_0 e^{-t/\tau} = -v(t)$$