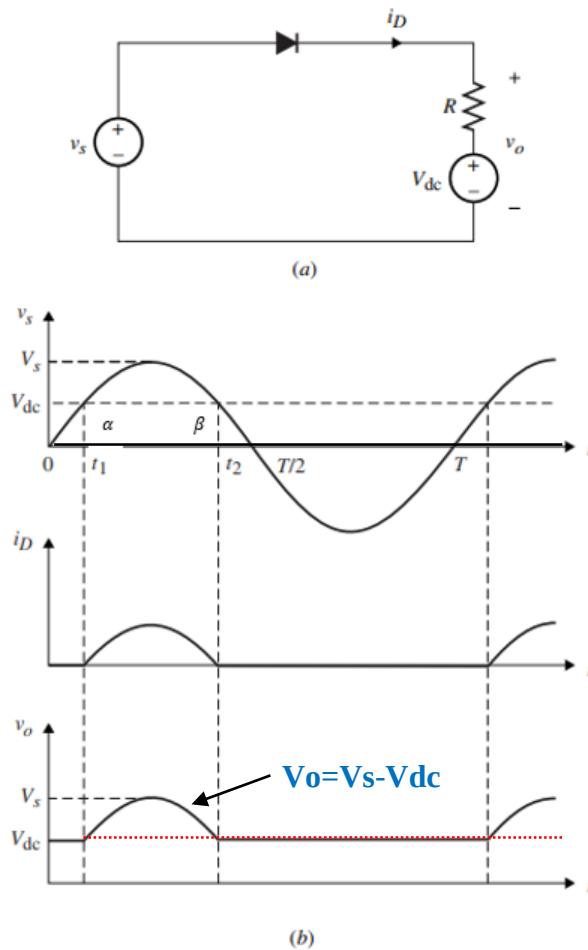


Lecture -3-

4) Half-wave Rectifier with (R load + DC Source)

- If the output is connected to a battery, the rectifier can be used as a battery charger. This is shown in Figure (a).
- diode D conducts (turn on) at $V_s > E$,
- diode D conducts (turn off) at $V_s < E$,



The angle α can be found from:

$$E = V_m \sin \alpha = V_{dc} \quad \rightarrow \rightarrow \rightarrow \rightarrow \rightarrow \quad \alpha = \sin^{-1} \left(\frac{E}{V_m} \right)$$

$$V_{o(load)} = \frac{1}{2\pi} \int_{\alpha}^{\beta} (V_m \sin wt - E) d(wt)$$

$$\begin{aligned}
&= \frac{1}{2\pi} \left[\int_{\alpha}^{\beta} (Vm \sin \omega t \cdot d(\omega t) - \int_{\alpha}^{\beta} E \cdot d(\omega t) \right] \\
&= \frac{1}{2\pi} \left([-Vm \cos \omega t]_{\alpha}^{\beta} - [E \omega t]_{\alpha}^{\beta} \right) \\
&= \frac{1}{2\pi} \left[-Vm (\cos \beta - \cos \alpha) - E(\beta - \alpha) \right] \\
&= \frac{1}{2\pi} \left[-Vm \cos \beta + Vm \cos \alpha - E\beta + E\alpha \right] \quad \text{at } \beta = \pi - \alpha \\
&= \frac{1}{2\pi} \left[-Vm \cos (\pi - \alpha) + Vm \cos \alpha - E(\pi - \alpha) + E\alpha \right]
\end{aligned}$$

for $\cos (\pi - x) = -\cos x$

$$= \frac{1}{2\pi} \left[Vm \cos \alpha + Vm \cos \alpha - \pi E + E\alpha + E\alpha \right]$$

$$V_{o(load)} = \frac{1}{2\pi} \left[2 Vm \cos \alpha + 2 E\alpha - \pi E \right]$$

$$I_{o(load)} = \frac{1}{2\pi R} \left[2 Vm \cos \alpha + 2 E\alpha - \pi E \right]$$

الاشتقاق مهم

$$V_{rms} = \sqrt{\frac{1}{2\pi} \int_{\alpha}^{\beta=\pi-\alpha} (V_m \sin \omega t - E)^2 d(\omega t)}$$

$$= \sqrt{\frac{1}{2\pi} \left[\left(\frac{V_m^2}{2} + E^2 \right) (\pi - 2\alpha) + \frac{V_m^2}{2} \sin 2\alpha - 4V_m E \cos \alpha \right]}$$

$$I_{rms} = \frac{V_{o,rms}}{R}$$

$$P_{R(resistor)} = I_{rms}^2 R; P_{battery} = P_{dc} = EI_{dc}$$

5) Half-wave Rectifier with (RL- load + DC Source)

Another variation of the half-wave rectifier is shown in Fig.a. The load consists of a resistance, an inductance, and a dc voltage. Starting the analysis at $\omega t = 0$ and assuming the initial current is zero, recognize that the diode will remain off as long as the voltage of the ac source is less than the dc voltage.

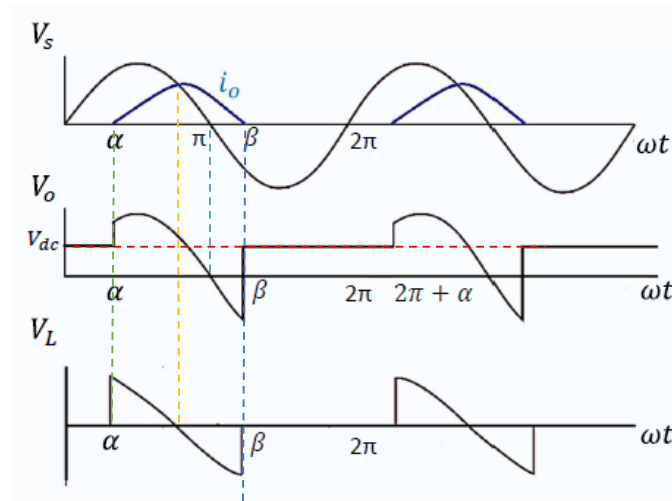
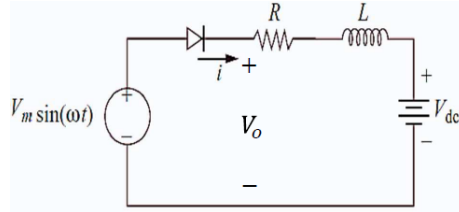


Figure (a) Half-wave rectifier with RL source load

$$V_m \sin(\omega t) = Ri(t) + L \frac{di(t)}{dt} + V_{dc}$$

$$i(t) = i_f(t) + i_n(t)$$

$$i_f(t) = \frac{V_m}{Z} \sin(\omega t - \theta) - \frac{V_{dc}}{R}$$

$$i_n(t) = Ae^{-t/\tau}$$

$$i_o(\omega t) = \begin{cases} \frac{V_m}{Z} \left[\sin(\omega t - \theta) - \frac{V_{dc}}{R} + Ae^{\left(\frac{-\omega t}{\omega \tau}\right)} \right] & \text{for } \alpha < \omega t < \beta \\ 0 & \text{otherwise} \end{cases}$$

where $A = \left[-\frac{V_m}{Z} \sin(\alpha - \theta) + \frac{V_{dc}}{R} \right] e^{\left(\frac{\alpha}{\omega \tau}\right)}$

The constant A is evaluated by using the initial condition for current $i(\alpha) = 0$

$$\text{where } Z = \sqrt{R^2 + (\omega L)^2} \quad \text{and} \quad \theta = \tan^{-1}\left(\frac{\omega L}{R}\right) \quad \tau = \frac{L}{R}$$

$$\begin{aligned} V_{o(load)} &= \frac{1}{2\pi} \left[\int_0^\alpha E \cdot d(\omega t) + \int_\alpha^\beta (Vm \sin \omega t \cdot d(\omega t)) + \int_\beta^{2\pi} E \cdot d(\omega t) \right] \\ &= \frac{1}{2\pi} [E\alpha + Vm (\cos \alpha - \cos \beta) + E(2\pi - \beta)] \\ &= \frac{1}{2\pi} [Vm (\cos \alpha - \cos \beta) + E(\alpha + 2\pi - \beta)] \end{aligned}$$

$$I_{o(load)} = \frac{V_{o(load)} - E}{R}$$

$$I_{o,avg} = \frac{1}{2\pi} \int_\alpha^\beta i_o(\omega t) d\omega t$$

$$I_{o,rms} = \sqrt{\frac{1}{2\pi} \int_\alpha^\beta i_o^2(\omega t) d\omega t}$$

$$P_R = I_{o,rms}^2 R, \quad P_{dc} = I_{o,avg} V_{dc}$$

$$P_{ac} = P_{dc} + P_R = I_{o,avg} V_{dc} + I_{o,rms}^2 R$$

$$PF = \frac{P}{S} = \frac{P_{ac}}{S}$$

Example:

For the half-wave rectifier with RL-Source Load, $R=2 \Omega$, $L=20 \text{ mH}$, and $V_{dc}=100 \text{ V}$. The ac source is 120 V rms at 60 Hz . Determine (a) an expression for the current in the circuit, (b) the power absorbed by the dc source, **$\beta = 3.37 \text{ rad (193}^\circ\text{)}$** .

■ Solution

From the parameters given,

$$V_m = 120\sqrt{2} = 169.7 \text{ V}$$

$$Z = [R^2 + (\omega L)^2]^{0.5} = 7.80 \Omega$$

$$\theta = \tan^{-1}(\omega L/R) = 1.31 \text{ rad}$$

$$\alpha = \sin^{-1}(100/169.7) = 36.1^\circ = 0.630 \text{ rad}$$

$$\omega\tau = 377(0.02/2) = 3.77 \text{ rad}$$

(a) Using Eq.

$$i_o(\omega t) = \begin{cases} \frac{V_m}{Z} \left[\sin(\omega t - \theta) - \frac{V_{dc}}{R} + A e^{\left(\frac{-\omega t}{\tau}\right)} \right] & \text{for } \alpha < \omega t < \beta \\ 0 & \text{otherwise} \end{cases}$$

$$\text{where } A = \left[-\frac{V_m}{Z} \sin(\alpha - \theta) + \frac{V_{dc}}{R} \right] e^{\left(\frac{\alpha}{\omega \tau}\right)}$$

$$A = \left[\left(\frac{120\sqrt{2}}{7.8} \right) \sin(0.63 - 1.31) + \frac{100}{2} \right] e^{\left(\frac{0.63}{3.77}\right)}$$

$$A = [-21.75 (-0.628) + 50] e^{0.167} = (63.659) e^{0.167} = 75.23$$

OR//

$$\theta = 1.32 * \frac{180}{\pi} = 75.05^\circ$$

$$A = \left[\left(\frac{120\sqrt{2}}{7.8} \right) \sin(36.1 - 75.05) + \frac{100}{2} \right] e^{\left(\frac{0.63}{3.77}\right)} = 75.3$$

$$i(\omega t) = 21.75 \sin(\omega t - 1.31) - 50 + 75.23 e^{\left(\frac{-\omega t}{3.77}\right)} \quad A$$

b) The power absorbed by the dc source is $I_o V_{dc}$.

$$\begin{aligned} V_{o(load)} &= \frac{1}{2\pi} [V_m (\cos \alpha - \cos \beta) + E(\alpha + 2\pi - \beta)] \\ &= \frac{1}{2\pi} [120 \sqrt{2} (\cos 0.63 - \cos 3.37) + E(0.63 + 2\pi - 3.37)] \\ &= \frac{1}{2\pi} [169.7(0.8 + 0.97) + 100(3.54)] = 104.146 \quad v \end{aligned}$$

$$I_{o(load)} = \frac{V_{o(load)} - E}{R} = \frac{104.146 - 100}{2} = 2.07 \quad A$$

$$P_{dc} = I_{o(load)} * V_{dc} = 2.07 * 100 = 207 \text{ w}$$