



Ministry of Higher Education and
Scientific Research
Tikrit University
Engineering Collage –Al shirqat



FUNDAMENTALS OF ELECTRICAL ENGINEERING

LECTURE 2

SERIES AND PARALLEL RESISTORS

PREPARED BY
TEACHING ASSISTANT

ABDULLAH AHMED ALWAN

Classroom: xtofyek4

المسائي Classroom: cftecvvp

General objectives

➤ Series Connection

- **Increases total resistance:** When resistors are connected in series, the total resistance increases, reducing the current flowing through the circuit.
- **Divides voltage:** The total voltage is divided among the components connected in series according to their resistance values.
- **Maintains constant current:** The same current flows through all components in a series connection.
- **Used in applications such as:** Voltage dividers, filter circuits, and circuit protection.

➤ Parallel Connection

- **Decreases total resistance:** When resistors are connected in parallel, the total resistance decreases, increasing the total current in the circuit.
- **Divides current:** The total current is divided among the parallel branches according to their resistance values.
- **Maintains constant voltage:** The voltage across all components in parallel remains the same.
- **Used in applications such as:** Increasing power capacity, load distribution, and minimizing power loss.

General objectives

➤ Voltage Divider

- **Reduces voltage to a specific level:** Used to generate a voltage lower than the total voltage as needed.
- **Provides reference signals:** Used in electronic circuits as a reference voltage source.
- **Used in applications such as:** Analog circuits, sensors, and measuring devices.

➤ Current Divider

- **Distributes current among branches:** It divides the current among multiple resistors connected in parallel.
- **Controls the current flowing through each branch:** Based on the resistance value of each path.
- **Used in applications such as:** DC circuits, filtering techniques, and measuring instruments.

Specific objectives:

➤ Series Connection

- Achieve a higher voltage at the same current.
- Distribute the total voltage across multiple electrical components.
- Maintain the same current in all elements connected in series.
- Improve the performance of systems requiring a higher voltage than a single source can provide.
- Increase the equivalent resistance of the circuit.

➤ Parallel Connection

- Achieve a higher current at the same voltage.
- Distribute the total current across multiple branches to prevent overload.
- Ensure circuit operation continues even if one component fails.
- Reduce the equivalent resistance of the circuit, increasing power transmission efficiency.

Specific objectives:

➤ Voltage Divider

- Reduce the voltage to a suitable level for different loads.
- Provide a reference voltage for control circuits and sensors.
- Protect sensitive components from high voltage.
- Simplify electronic circuits requiring different voltage levels.

➤ Current Divider

- Distribute current among multiple branches in a circuit.
- Reduce the current in each branch to protect components from overloading.
- Improve energy consumption efficiency in electrical circuits.
- Used in measurement and control circuits to determine the appropriate current for each element.

Series Resistors and Voltage Division

The **equivalent resistance** of any number of resistors connected in series is the sum of the individual resistances.

For N resistors in series then

Resistance :
$$R_{eq} = R_1 + R_2 + \cdots + R_N = \sum_{n=1}^N R_n$$

$$R_{eq} = R_1 + R_2$$

Voltage :

$$v = v_t = v_1 + v_2$$

Current :

$$i = i_t = i_1 = i_2$$

$$i = i_t = \frac{v_t}{R_{eq}}$$

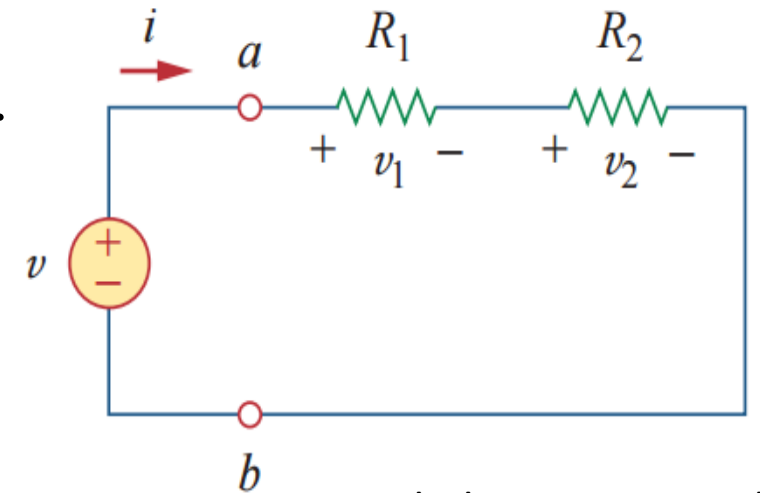


Figure 3-1 A single-loop circuit with two resistors in series.


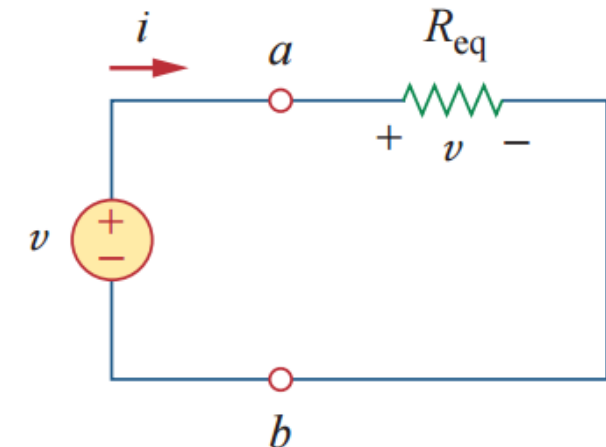


Figure 3-2 Equivalent circuit of the Fig. 3.1 circuit

Series Resistors and Voltage Division

$$v_1 = \frac{R_1}{R_1 + R_2} v, \quad v_2 = \frac{R_2}{R_1 + R_2} v$$
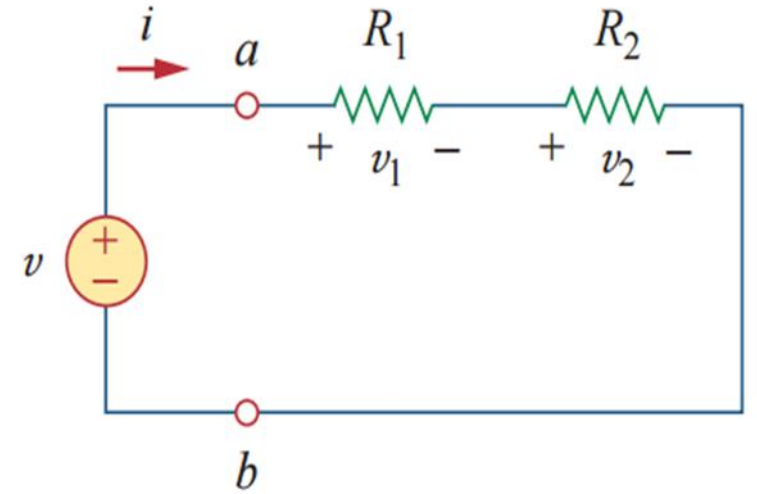
$$v_x = v \times \left(\frac{R_x}{R_1 + R_2} \right)$$



Parallel Resistors and Current Division

The **equivalent resistance** of two parallel resistors is equal to the product of their resistances divided by their sum.

the general case of a circuit with N resistors in parallel.

The equivalent resistance is

Resistance :

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N}$$

where R_{eq} is the equivalent resistance of the resistors in parallel:

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

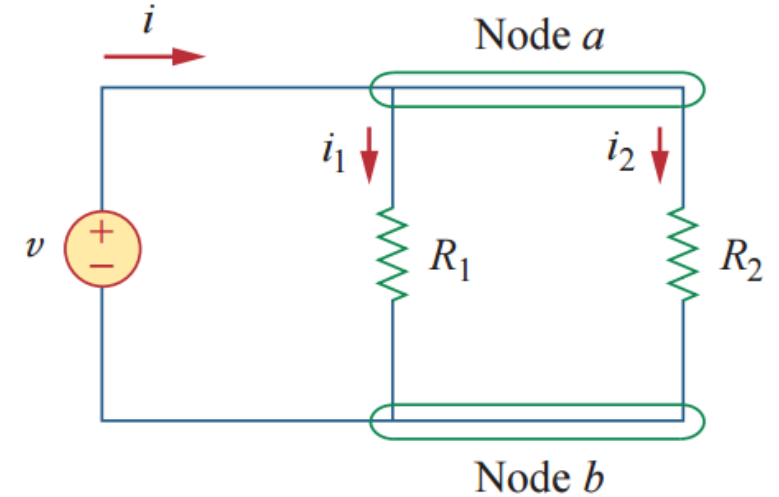


Figure 3-3 A single-loop circuit with two resistors in parallel.

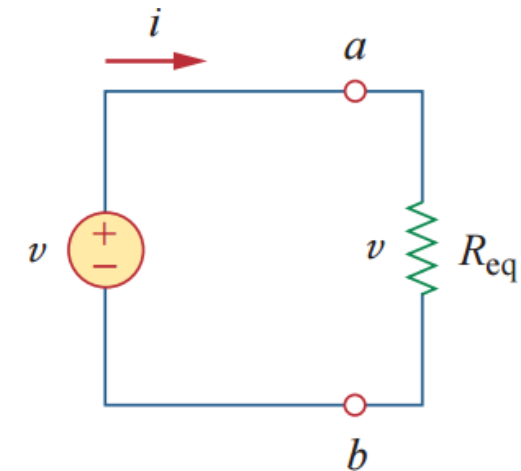


Figure 3-4 Equivalent circuit of the Fig. 3.3 circuit

Parallel Resistors and Current Division

Voltage :


$$v = v_t = v_1 = v_2 = i_t \times R_{eq} = i_1 R_1 = i_2 R_2$$

Current :

$$i = i_t = i_1 + i_2$$

$$i_1 = i_t \times \left(\frac{R_2}{R_1 + R_2} \right)$$

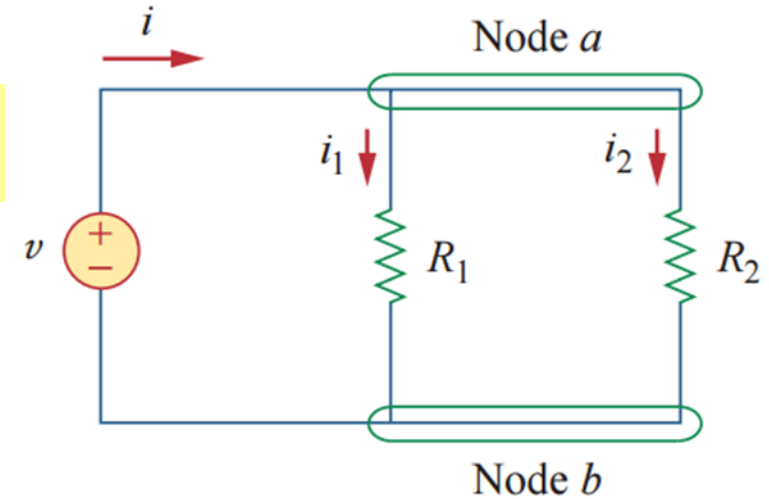
$$i_2 = i_t \times \left(\frac{R_1}{R_1 + R_2} \right)$$



$$i = i_t = \frac{v_t}{R_{eq}}$$

Wye-Delta Transformations

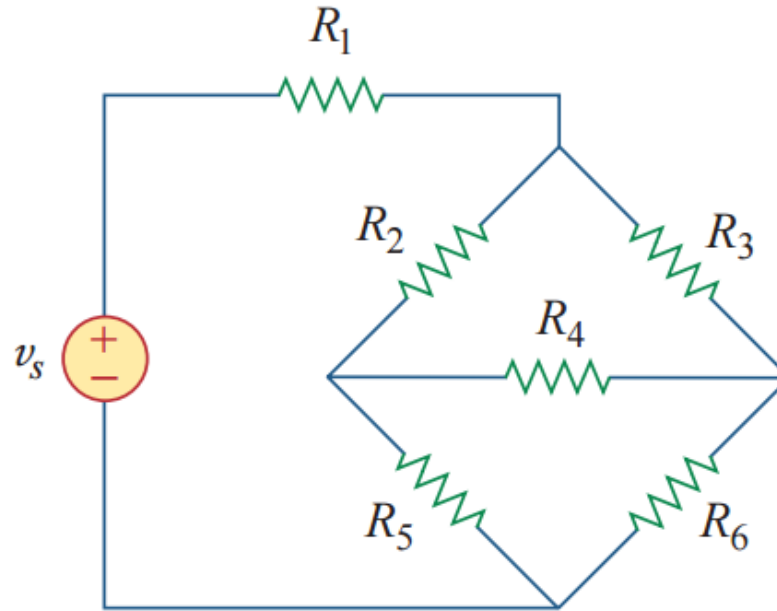Situations often arise in circuit analysis when the resistors are neither in parallel nor in series. For example, consider the bridge circuit as shown in figure below:



In this circuit R_1, R_2, R_3, R_4, R_5 and R_6 are neither in parallel nor in series.

Question :When to convert **delta** → **star** or vice versa?

- ✓ **Delta** → **Star**: Used when reducing starting current or lowering the voltage on windings is needed. This is common in motor starting applications to reduce the inrush current.
- ✓ **Star** → **Delta**: Used when operating equipment at full power after startup or when a higher voltage is required. This is typically seen in star-delta starters for motors, where the motor starts in the star configuration (low voltage) and then switches to delta (full voltage) for normal operation.

Wye-Delta Transformations

These are the wye (**Y**) or tee (**T**) network shown in Fig. 3.8 and the delta (Δ) or pi (π) network shown in Fig. 3.9

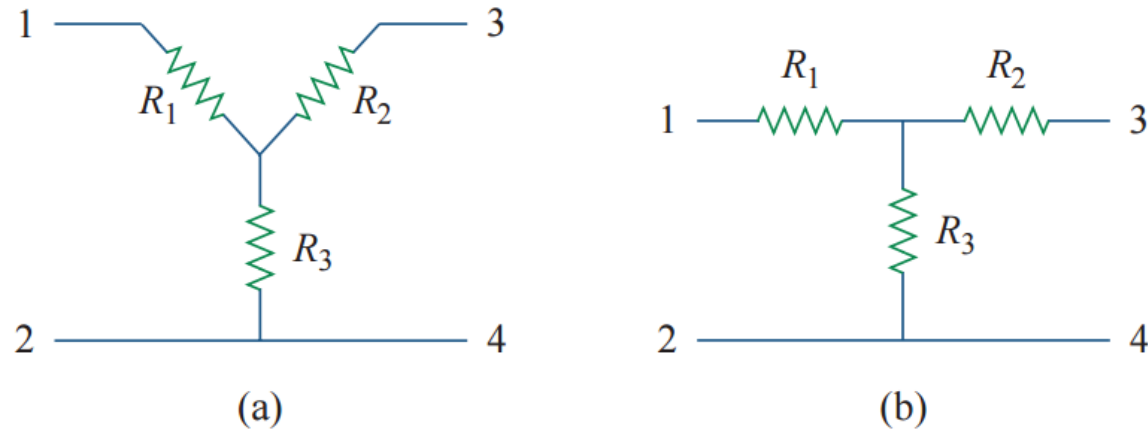


Figure 3-8 Two forms of the same network: (a) **Y** ,(b) . **T**.

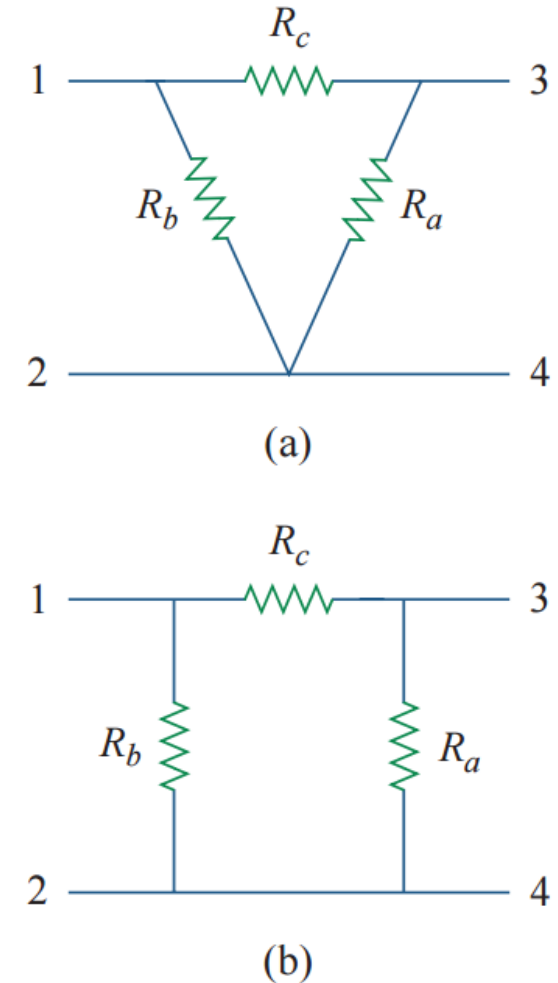


Figure 3-9 Two forms of the same network: (a) Δ ,(b) . π .

Delta to Wye Conversion

Each resistor in the Y network is the product of the resistors in the two adjacent Δ branches, divided by the sum of the three Δ resistors.

$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c}$$

$$R_2 = \frac{R_c R_a}{R_a + R_b + R_c}$$

$$R_3 = \frac{R_a R_b}{R_a + R_b + R_c}$$

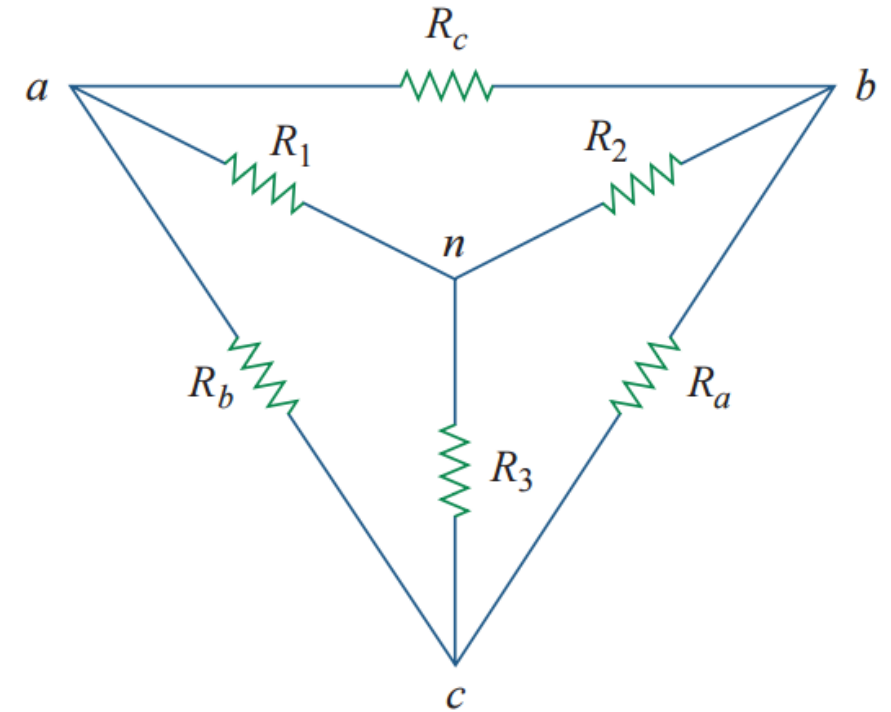


Figure 3-10 Superposition of Y and Δ networks as an aid in transforming one to the other

Wye to Delta Conversion

Each resistor in the Δ network is the sum of all possible products of Y resistors taken two at a time, divided by the opposite Y resistor.

$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$

$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$

$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$

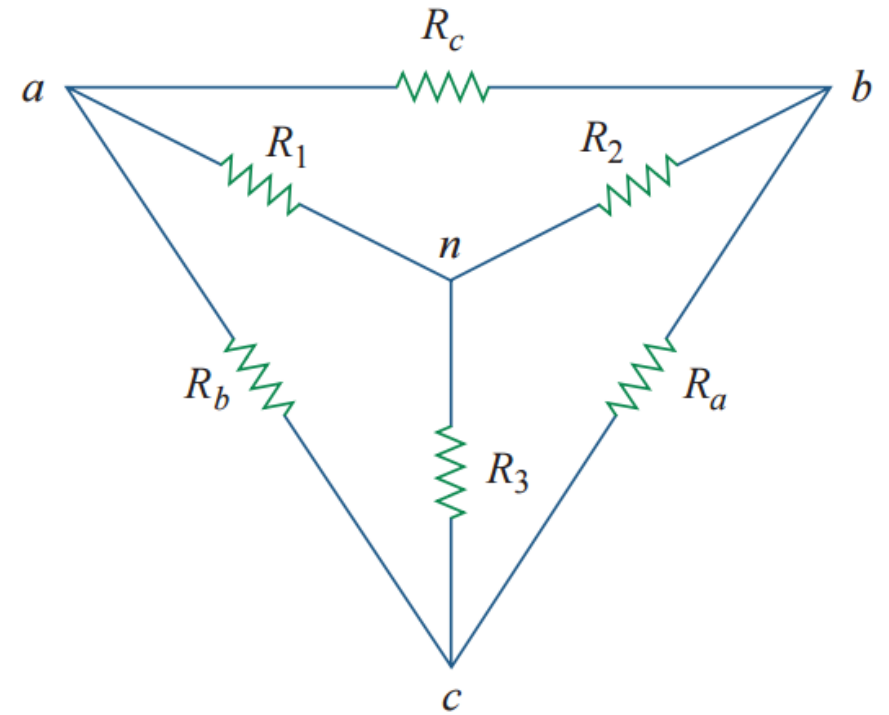


Figure 3-10 Superposition of Y and Δ networks as an aid in transforming one to the other

Wye-Delta Transformations

➤Note :-

- The **Y** and Δ network are said to be **balanced** when :

$$R_1=R_2=R_3$$

And

$$R_a=R_b=R_c$$

- Under balance condition, the convention equations become:

$$R_{\mathbf{Y}} = \frac{R_{\Delta}}{3}$$

$$V_{\mathbf{Y}} = \frac{V_{\Delta}}{\sqrt{3}}$$

$$R_{\Delta} = 3R_{\mathbf{Y}}$$

EX: Find the total resistance of the network of Figure below where $R_A = 3\Omega$, $R_B = 3\Omega$, and $R_C = 6\Omega$.

Solution:

$$R_1 = \frac{R_B R_C}{R_A + R_B + R_C} = \frac{(3\Omega)(6\Omega)}{3\Omega + 3\Omega + 6\Omega} = \frac{18\Omega}{12} = 1.5\Omega \leftarrow$$

$$R_2 = \frac{R_A R_C}{R_A + R_B + R_C} = \frac{(3\Omega)(6\Omega)}{12\Omega} = \frac{18\Omega}{12} = 1.5\Omega \leftarrow$$

$$R_3 = \frac{R_A R_B}{R_A + R_B + R_C} = \frac{(3\Omega)(3\Omega)}{12\Omega} = \frac{9\Omega}{12} = 0.75\Omega$$

Two resistors of the Δ were equal; therefore, two resistors of the Y will be equal.



Replacing the Δ by the Y, as shown in Fig.

$$R_T = 0.75\Omega + \frac{(4\Omega + 1.5\Omega)(2\Omega + 1.5\Omega)}{(4\Omega + 1.5\Omega) + (2\Omega + 1.5\Omega)}$$

$$= 0.75\Omega + \frac{(5.5\Omega)(3.5\Omega)}{5.5\Omega + 3.5\Omega}$$

$$= 0.75\Omega + 2.139\Omega$$

$$R_T = 2.889\Omega$$

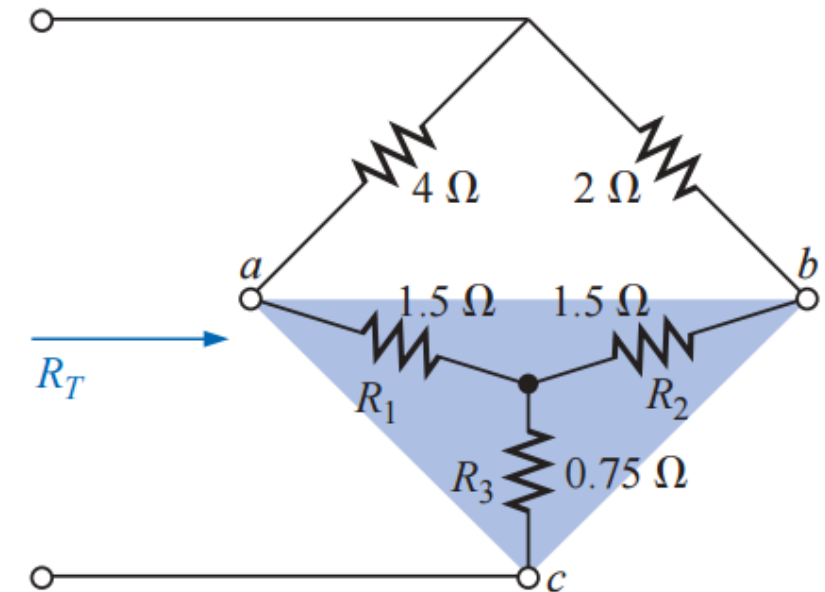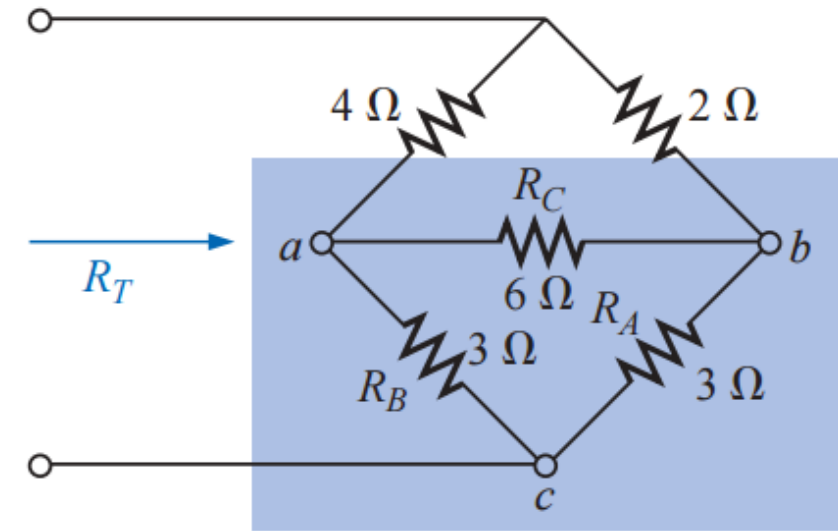

EX: Find the current (I) for the circuit shown in figure below.

Solution: $I = \frac{E}{R_{eq}}$

If we convert the (Y) network comprising (5 Ω , 10 Ω and 20 Ω) resistors, then:

$$R_a = \frac{5 * 10 + 10 * 20 + 20 * 5}{20} = \frac{350}{20} = 17.5 \Omega$$



$$R_b = \frac{350}{5} = 70 \Omega$$

$$R_c = \frac{350}{10} = 35 \Omega$$

$$12.5 \parallel 17.5 = \frac{12.5 * 17.5}{12.5 + 17.5} = 7.292 \Omega$$

$$15 \parallel 35 = \frac{15 * 35}{15 + 35} = 10.5 \Omega$$
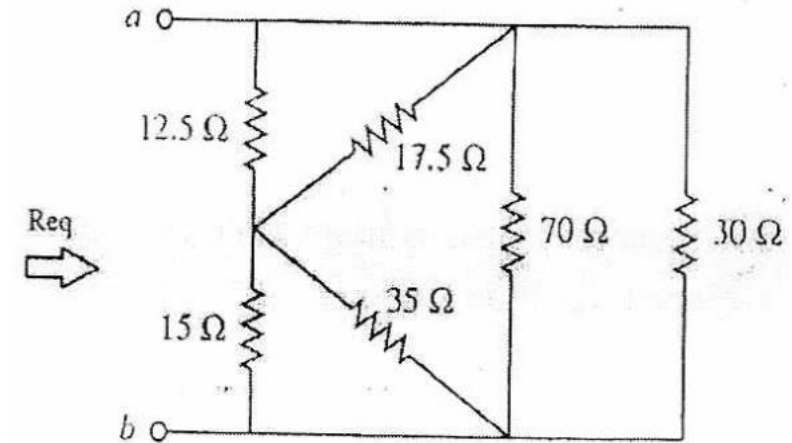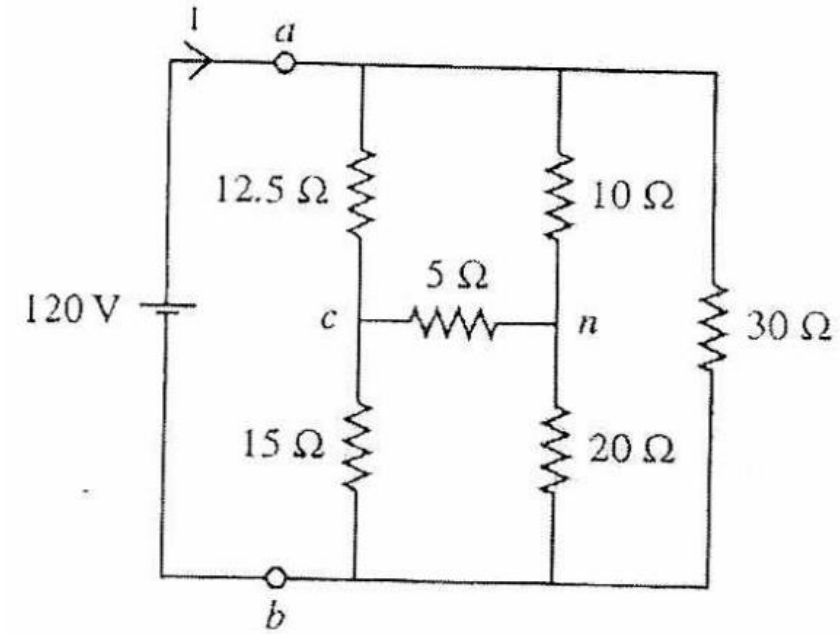
$$70 \parallel 30 = \frac{70 * 30}{70 + 30} = 21 \Omega$$



$$\therefore R_{eq} = (7.292 + 10.5) \parallel 21 = \frac{17.792 * 21}{17.792 + 21} = 9.632 \Omega$$

$$\therefore I = \frac{12}{9.632} = 12.458 A$$

